

MC44608 SMPS Featuring Very Low Standby Power Consumption and Wide Range Output Voltage


Prepared by: Jan Grulich
ON Semiconductor Central Lab
Roznov, CZ



ON Semiconductor™

<http://onsemi.com>

APPLICATION NOTE

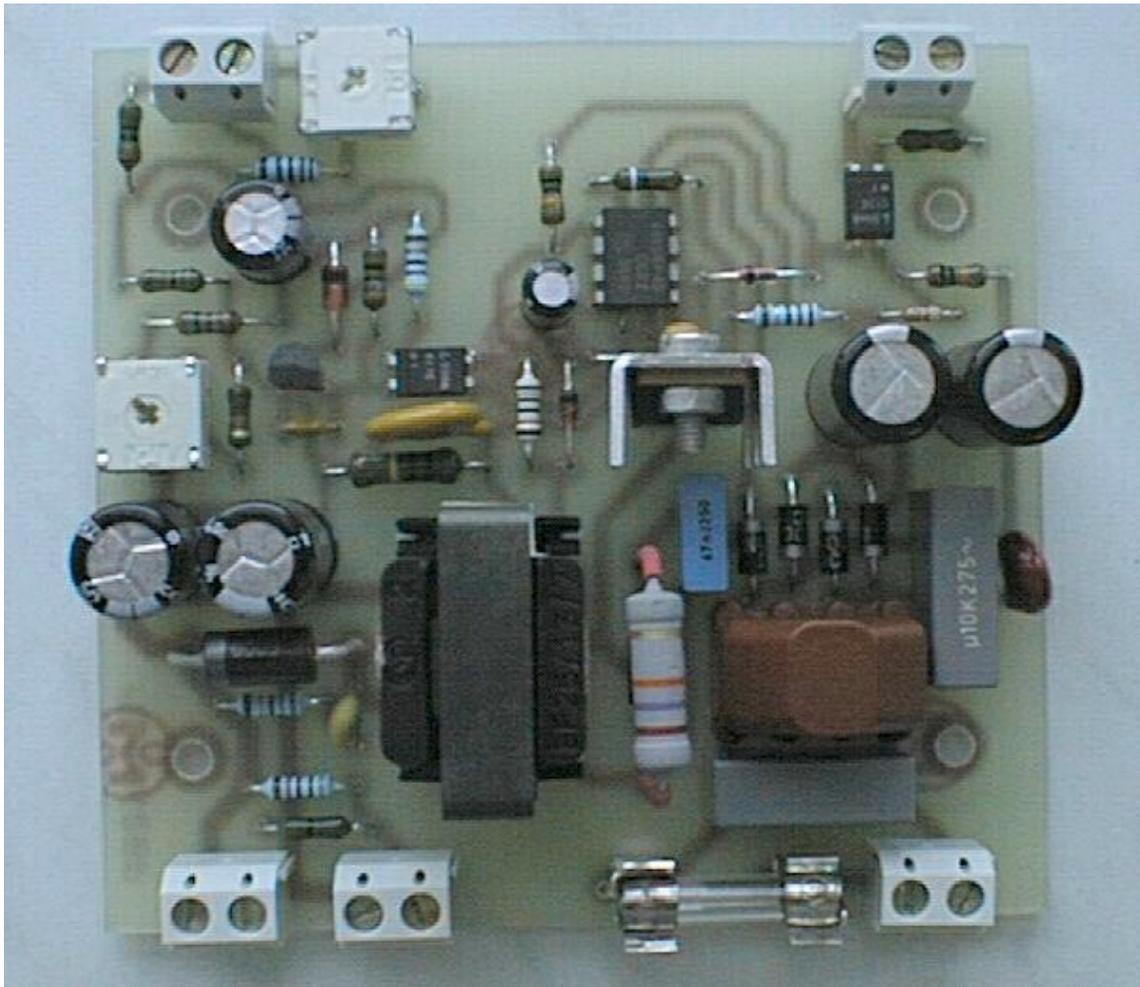

As it is well known, according to power saving regulations, we need to obtain a very low power consumption during standby condition for all equipment continuously powered on the mains. For “not saving” version of power supply, the standby power consumption is around 9.0 W (for 100 W power output). When using the MC44608 GreenLine™ Power supply controller, we obtain 1.3 W in standby mode. The result is absolutely phenomenal, but still, for some special applications, the

power reduction is not enough. In this case the only possibility to obtain a lower consumption in standby is to use a separate low output power supply (< 1.0 W) for powering only the microprocessor and switch off the rest of the application. The MC44608 is basically not designed for that use. However this is achievable by adding a few more components to the typical application schematic. In this case we can reach a standby power consumption as low as 200 mW.

AND8034/D

This result largely over passes the today standby power saving recommendations, meeting the 2005 recommendation limits.

Final price cost of additional components is below then 0.5 US\$ and the total price of this power supply remains the same, compared to typical application circuitry, since all components dealing with the reconfiguration of secondary side can be removed.

The basic idea to reach this performance is to power the IC in the phase, in which it has the lowest power consumption. At the same time is necessary to stop the operation of the output stage and leave IC in steady state conditions. In this case the secondary side output reconfiguration topology is not used.

Schematic of whole SMPS is presented in Figure 1.

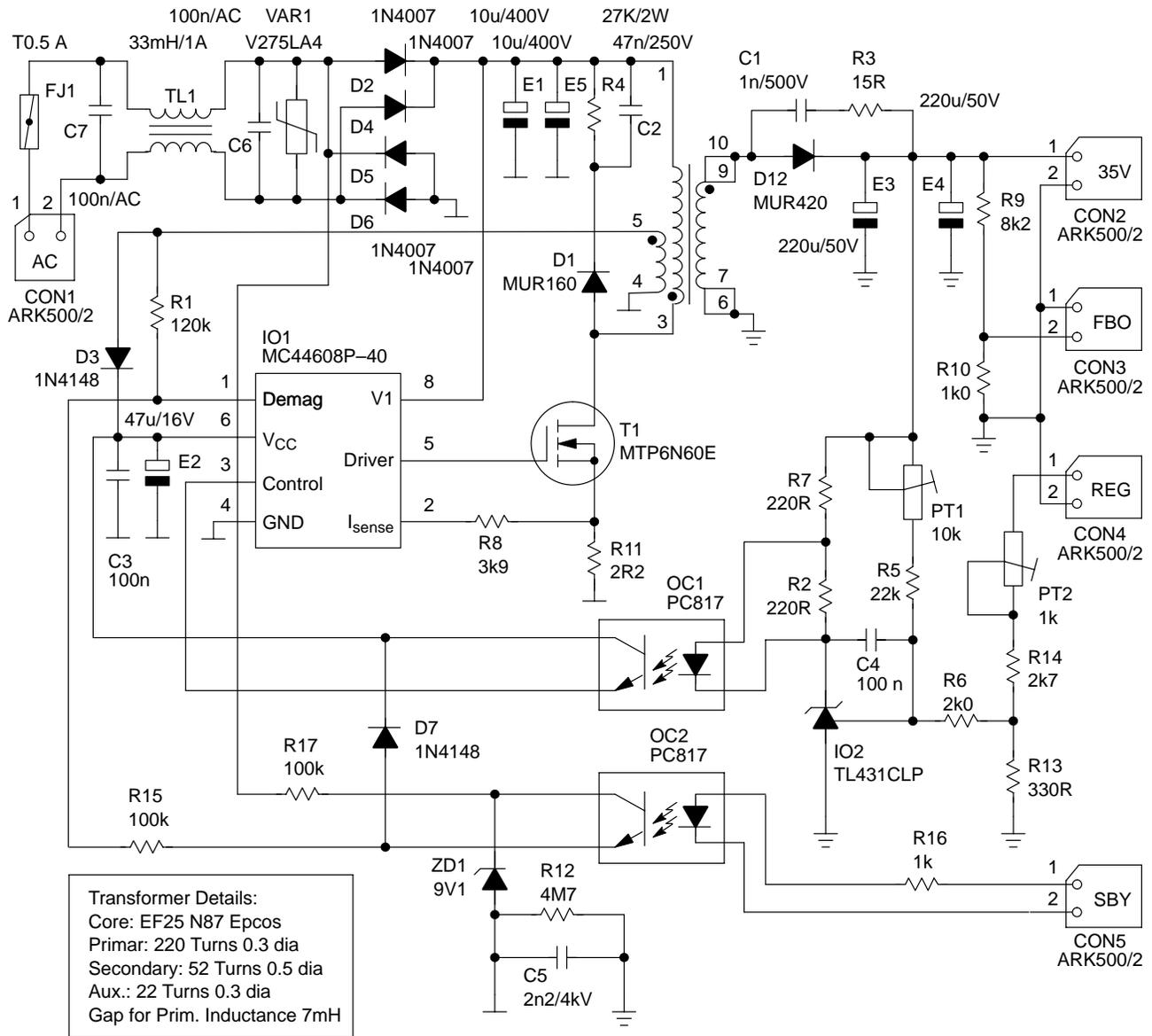


Figure 1. Schematic of SMPS

AND8034/D

As shown in Figure 1, the schematic includes all components to build a real application: safety fuse, input EMI filter, over voltage protection and rectifier, two filtering capacitors (2 capacitors for smaller ESR and therefore lower the EMI radiation). The power switch used here is the MTP6N60E. A standard RDC clamp in parallel with the primary winding is used as a spike protection. At the source of power switch a current sensing resistor R11 leads the signal to I_{sense} pin of the IC through R8. The aux. winding of the transformer is used to power the V_{cc} pin of the IC and also provides demagnetization information. On the secondary winding the diode D12 supplies energy for secondary load. This diode is protected against voltage spikes by RC series combination (C1, R3). This voltage is used to feed control loop through the opto coupler OC1. This regulation is based on standard shunt regulator using monolithic TL431CLP.

To put the SMPS in standby mode a simple circuit (OC2, R16, R15, D7, ZD1) is added. When a 5.0 V logic signal is present on the standby connector, through the opto coupler OC2 a signal feeds the demag input of control IC. This causes a permanent stop of output signal and no more energy is transferred. The V_{cc} pin of the IC is now supplied through R17 and D7. The V_{cc} is maintained at a voltage higher 6.5 V and below 10 V. The IC remains in a latched off phase. The total consumption in this case is well below 200 mW.

We add an additional feature to drive the output voltage from a microcomputer.

Potentiometer PT2, R13, R14, R6 feed the control loops. R9 and R10 send the correction information to the microcomputer. Output voltage range and gain of control signal are adjustable by potentiometers PT1 and PT2.

In the table below are summarized measured values:

Input Voltage	Input Power	Output Power	Efficiency
200 V	20.0 W	16.3 W	81.5%
230 V	20.0 W	16.3 W	81.5%
260 V	20.0 W	16.3 W	81.5%
For maximal output power			
230 V	22.8 W	19.6 W	85.9%

The plots below show some waveforms at critical test points:

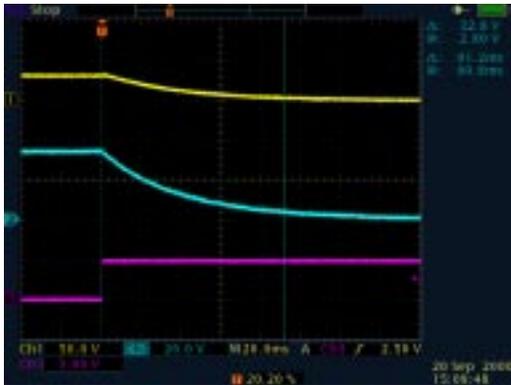


Figure 2. Output Voltage After Switch Off

Trace 1: Voltage at cathode of TL431CLP
Trace 2: Output voltage
Trace 3: Control signal for standby

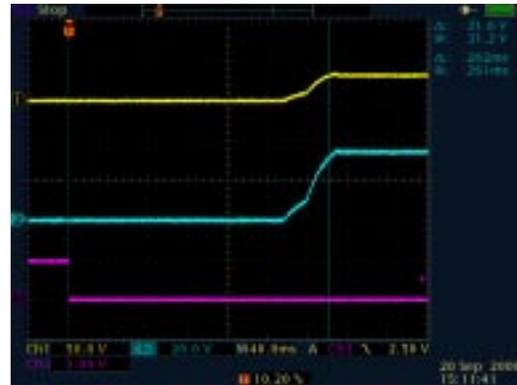


Figure 3. Output Voltage After Switch On

Trace 1: Voltage at cathode of TL431CLP
Trace 2: Output voltage
Trace 3: Control signal for standby

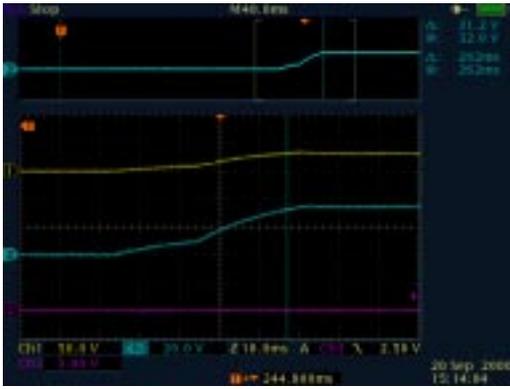


Figure 4. Zoomed Rising Edge of Figure 3

Trace 1: Voltage at cathode of TL431CLP
Trace 2: Output voltage
Trace 3: Control signal for standby

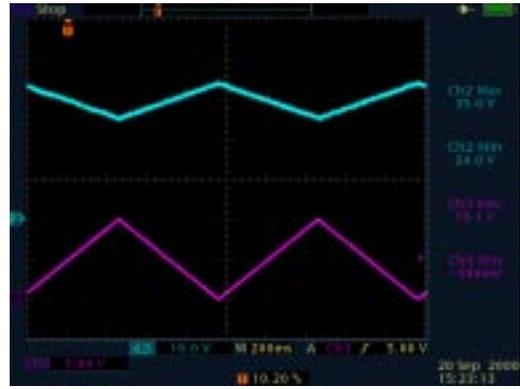


Figure 5. Output Voltage Regulation

Trace 2: Output voltage
Trace 3: Control signal for voltage regulation

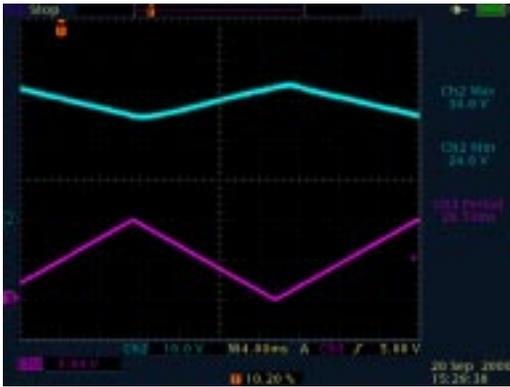


Figure 6. Minimal Period of Regulation

Trace 2: Output voltage
Trace 3: Control signal for voltage regulation

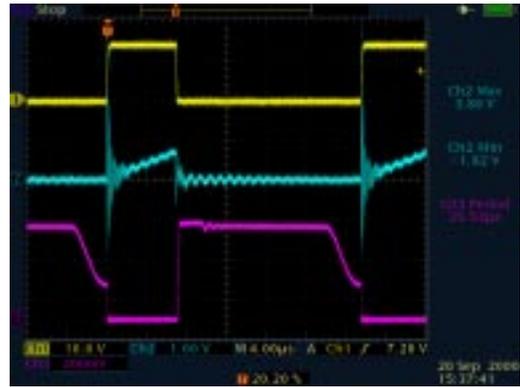


Figure 7. Primary Side Waveforms

Trace 1: Voltage at gate of power switch
Trace 2: Drain current of power switch
Trace 3: Drain voltage of power switch

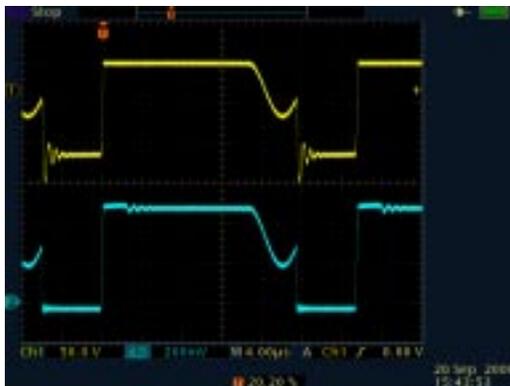


Figure 8. Switching Waveforms

Trace 1: Voltage at pin 10 of transformer
Trace 2: Voltage at pin 3 of transformer

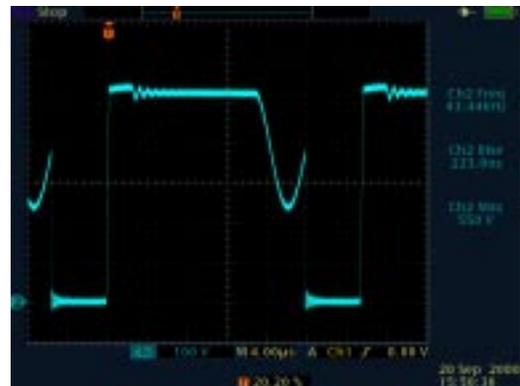


Figure 9. Primary Side Waveform

Trace 2: Detailed drain voltage of power switch

Notes

Notes

Notes

GreenLine is a trademark of Motorola, Inc.

ON Semiconductor and  are trademarks of Semiconductor Components Industries, LLC (SCILLC). SCILLC reserves the right to make changes without further notice to any products herein. SCILLC makes no warranty, representation or guarantee regarding the suitability of its products for any particular purpose, nor does SCILLC assume any liability arising out of the application or use of any product or circuit, and specifically disclaims any and all liability, including without limitation special, consequential or incidental damages. "Typical" parameters which may be provided in SCILLC data sheets and/or specifications can and do vary in different applications and actual performance may vary over time. All operating parameters, including "Typicals" must be validated for each customer application by customer's technical experts. SCILLC does not convey any license under its patent rights nor the rights of others. SCILLC products are not designed, intended, or authorized for use as components in systems intended for surgical implant into the body, or other applications intended to support or sustain life, or for any other application in which the failure of the SCILLC product could create a situation where personal injury or death may occur. Should Buyer purchase or use SCILLC products for any such unintended or unauthorized application, Buyer shall indemnify and hold SCILLC and its officers, employees, subsidiaries, affiliates, and distributors harmless against all claims, costs, damages, and expenses, and reasonable attorney fees arising out of, directly or indirectly, any claim of personal injury or death associated with such unintended or unauthorized use, even if such claim alleges that SCILLC was negligent regarding the design or manufacture of the part. SCILLC is an Equal Opportunity/Affirmative Action Employer.

PUBLICATION ORDERING INFORMATION

NORTH AMERICA Literature Fulfillment:

Literature Distribution Center for ON Semiconductor
 P.O. Box 5163, Denver, Colorado 80217 USA
Phone: 303-675-2175 or 800-344-3860 Toll Free USA/Canada
Fax: 303-675-2176 or 800-344-3867 Toll Free USA/Canada
Email: ONlit@hibbertco.com
 Fax Response Line: 303-675-2167 or 800-344-3810 Toll Free USA/Canada

N. American Technical Support: 800-282-9855 Toll Free USA/Canada

EUROPE: LDC for ON Semiconductor – European Support

German Phone: (+1) 303-308-7140 (Mon-Fri 2:30pm to 7:00pm CET)
Email: ONlit-german@hibbertco.com
French Phone: (+1) 303-308-7141 (Mon-Fri 2:00pm to 7:00pm CET)
Email: ONlit-french@hibbertco.com
English Phone: (+1) 303-308-7142 (Mon-Fri 12:00pm to 5:00pm GMT)
Email: ONlit@hibbertco.com

EUROPEAN TOLL-FREE ACCESS*: 00-800-4422-3781
 *Available from Germany, France, Italy, UK, Ireland

CENTRAL/SOUTH AMERICA:

Spanish Phone: 303-308-7143 (Mon-Fri 8:00am to 5:00pm MST)
Email: ONlit-spanish@hibbertco.com

ASIA/PACIFIC: LDC for ON Semiconductor – Asia Support

Phone: 303-675-2121 (Tue-Fri 9:00am to 1:00pm, Hong Kong Time)
Toll Free from Hong Kong & Singapore:
001-800-4422-3781
Email: ONlit-asia@hibbertco.com

JAPAN: ON Semiconductor, Japan Customer Focus Center
 4-32-1 Nishi-Gotanda, Shinagawa-ku, Tokyo, Japan 141-0031

Phone: 81-3-5740-2700
Email: r14525@onsemi.com

ON Semiconductor Website: <http://onsemi.com>

For additional information, please contact your local Sales Representative.